
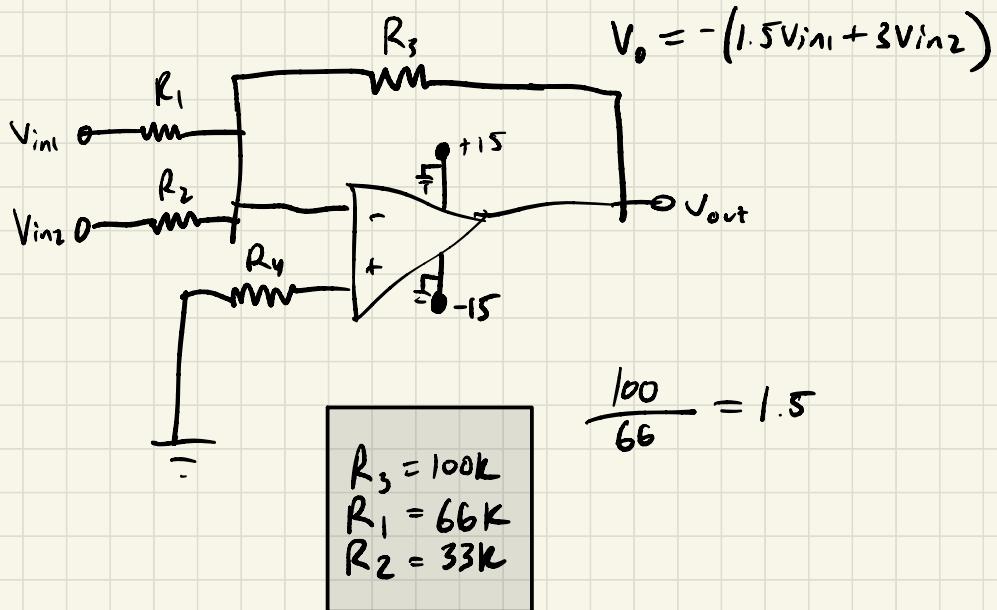


Lab 3: operational Amplifier circuits

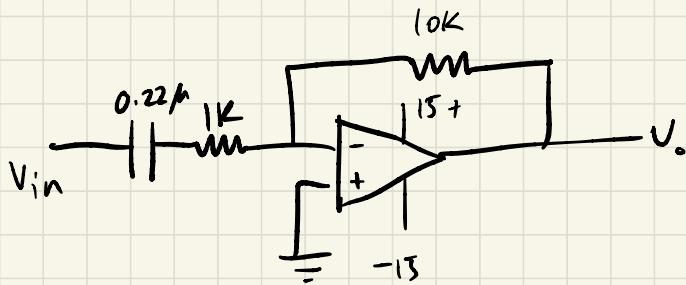

Transfer function :



$$R_y = \frac{1}{\frac{1}{100} + \frac{1}{33} + \frac{1}{66}} = 18\text{K}\Omega$$

PART 1:

a) R_1 = two $33\text{k}\Omega$ in series

$R_2 = 33\text{k}\Omega$ $R_3 = 10\text{k}$ and 8k in series


$R_3 = 100\text{k}\Omega$

Actual Value	Measured
$R_1 = 66\text{k}\Omega$	$65.663\text{ k}\Omega$
$R_2 = 33\text{k}\Omega$	$32.683\text{ k}\Omega$
$R_3 = 100\text{k}\Omega$	$99.205\text{k}\Omega$
$R_y = 18\text{k}\Omega$	$18.011\text{k}\Omega$
Capacitor	Capacitor
$C_1 = 0.1\mu\text{F}$	93.91nF
$C_2 = 0.1\mu\text{F}$	93.01nF


Expected Value	Measured
$V_{out} = -(1.5(3) + 3(3)) = -13.5$	-12.5V (Potential saturation)
$V_{out} = -(1.5(1) + 3(1)) = -4.5$	-4.5372V
$V_{out} = -(1.5(2) + 3(2)) = -9$	-9.0822V

b)

Built this circuit:

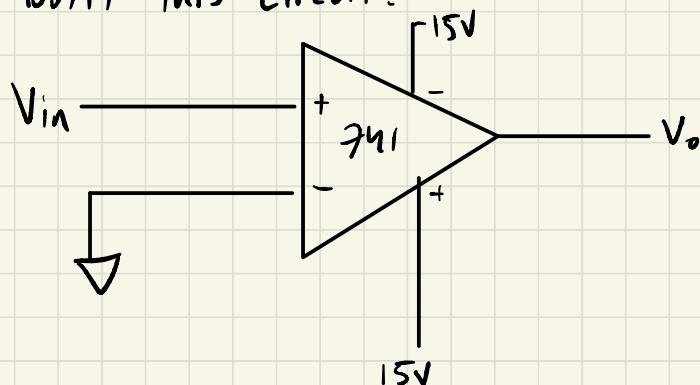


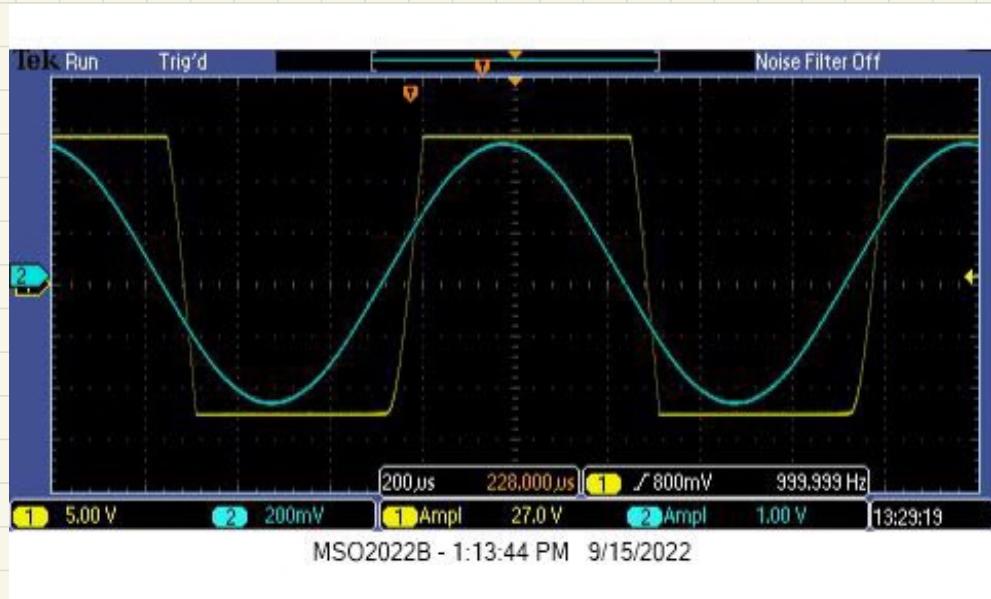Applied a 1kHz, 1Vp-p Sine Wave Signal to the Non-inverting input. This is what we got as our input and Output Signals.




Does the output change if 0.1V p-p?

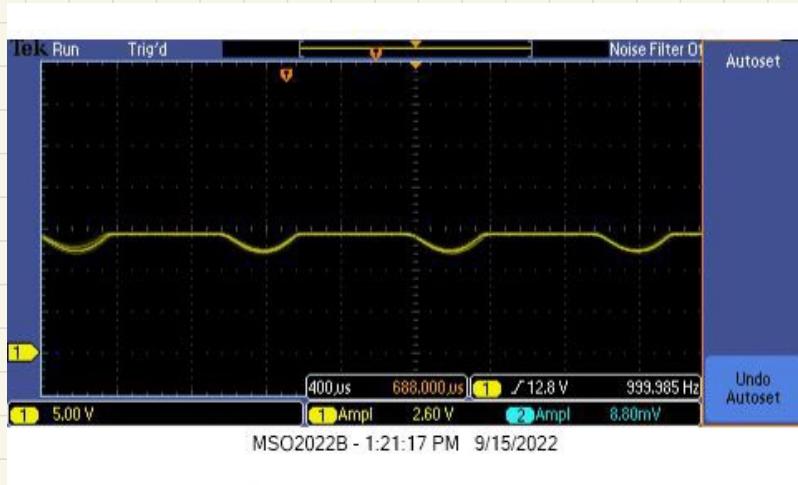yes the output does change, the output is a different looking wave that is less saturated. This is what it looked like.




What happens if the inverting input and non inverting is swapped

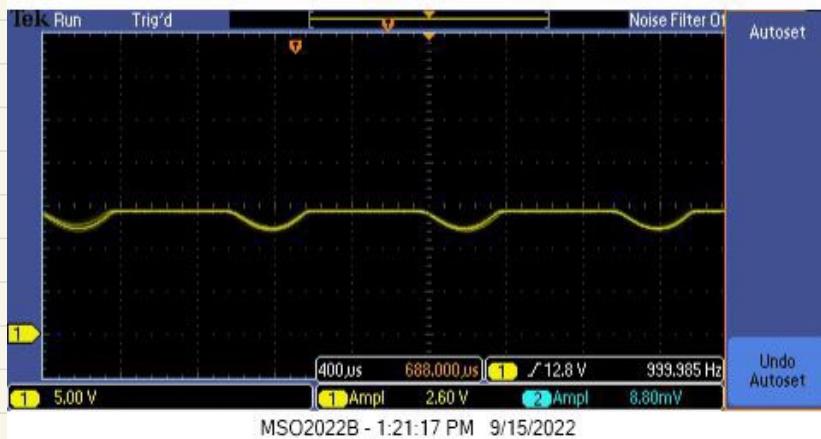
The Signal does not change after Swapping the inverting and Non inverting inputs.




c) Same Signal Applied to this circuit

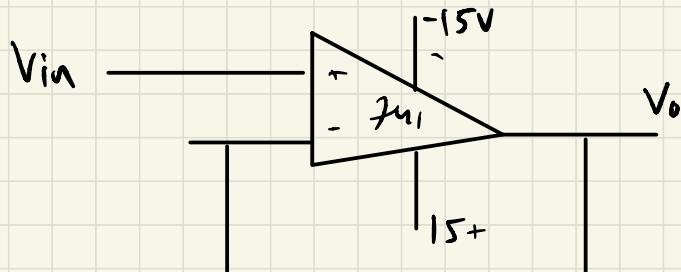

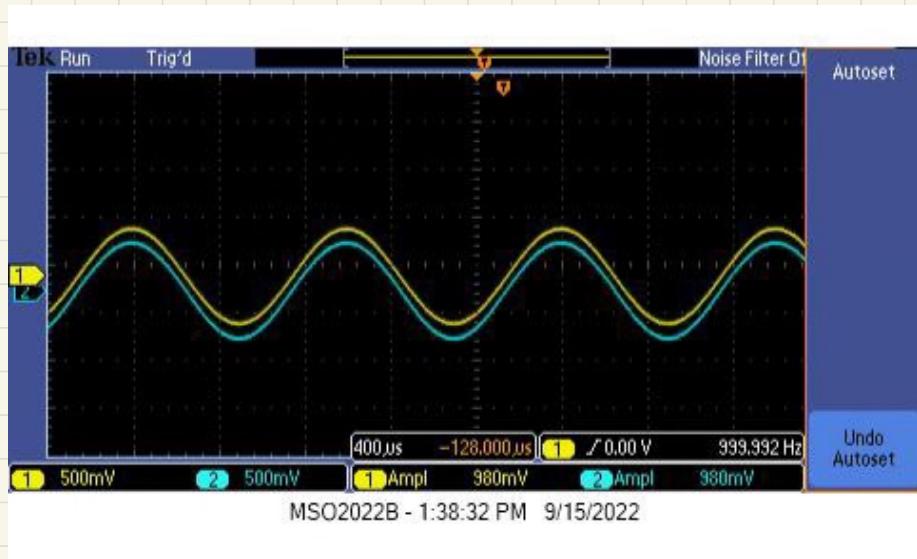It appears that the input and output signal are the same.



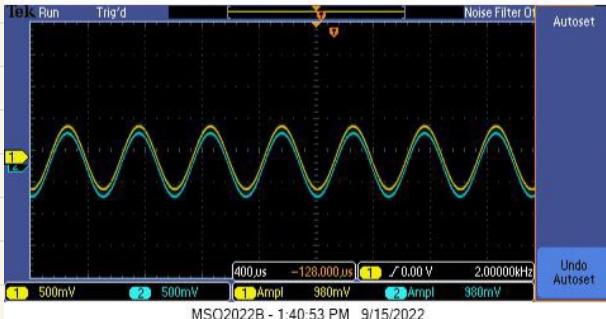We increased the input signal to 2kHz and Both inputs and outputs are identical.



What is the 3dB frequency?


You cannot get the 3dB frequency because both waves are identical

What is the input Resistance of the follower?


Infinity, because the nature of this circuit, also there are no resistors.

d)

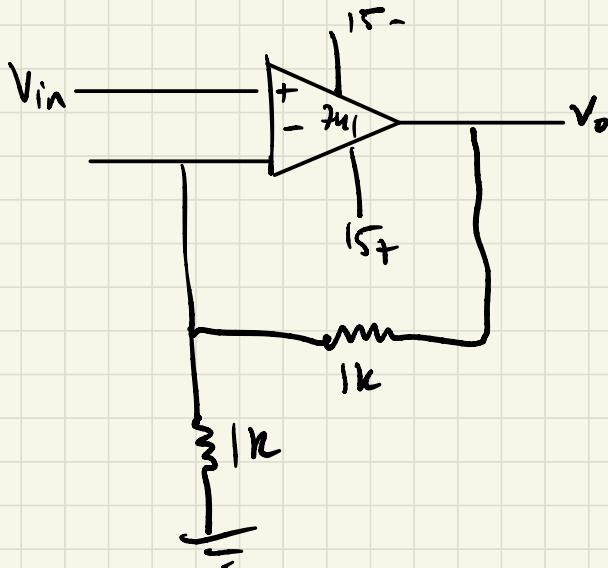The circuit below was created. The same input Voltage as part B was used-



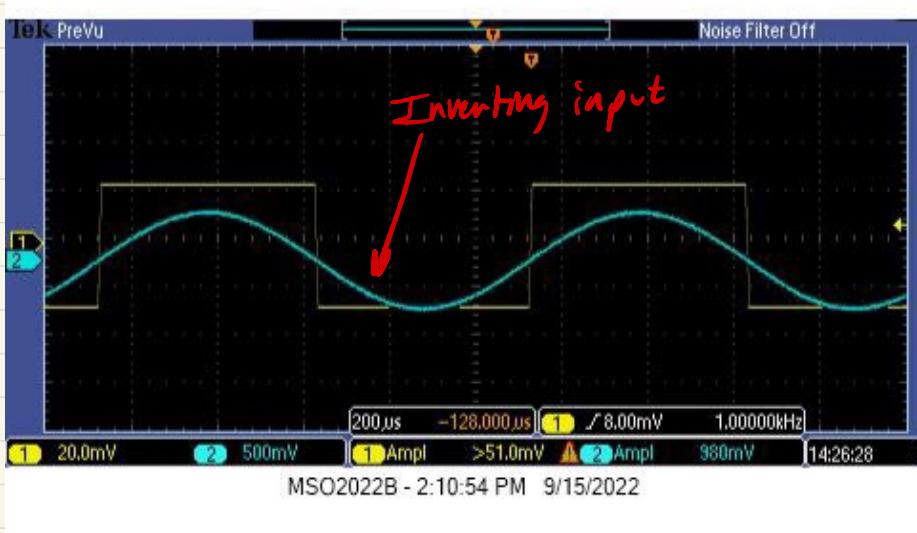The input (Blue wave), and output (yellow wave), are shown below



What is the voltage gain of the amp?

$$V_o = V_i \left(1 + \frac{R_2}{R_1} \right)$$

$$V_o = 1 + \frac{1000}{1000} = 2 \quad \text{Voltage gain} = 2$$

What happens when the amplitude of the input signal is too large?
The output stops being a square wave


What do you need to do to have a voltage gain of 10?

Change the value of R_2 and R_1 , such that...


$$\frac{R_2}{R_1} = 10.$$

e) The circuit shown below was built. A $1V_{p-p}$ triangular wave was inputted, The output waveform is then captured for 100Hz , 500Hz , 700Hz , 1kHz , and 10kHz .


100Hz

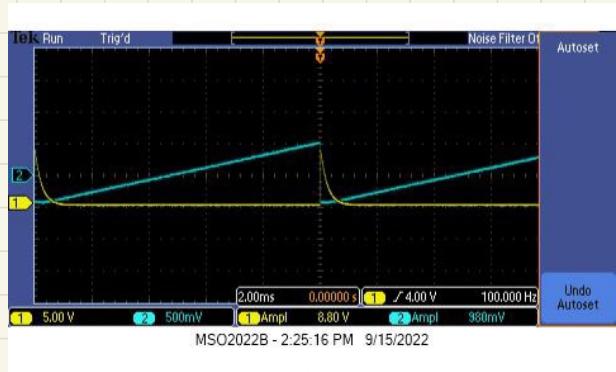


500Hz

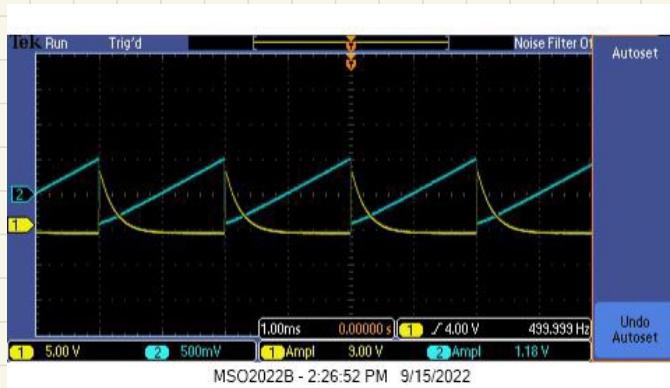


700 Hz

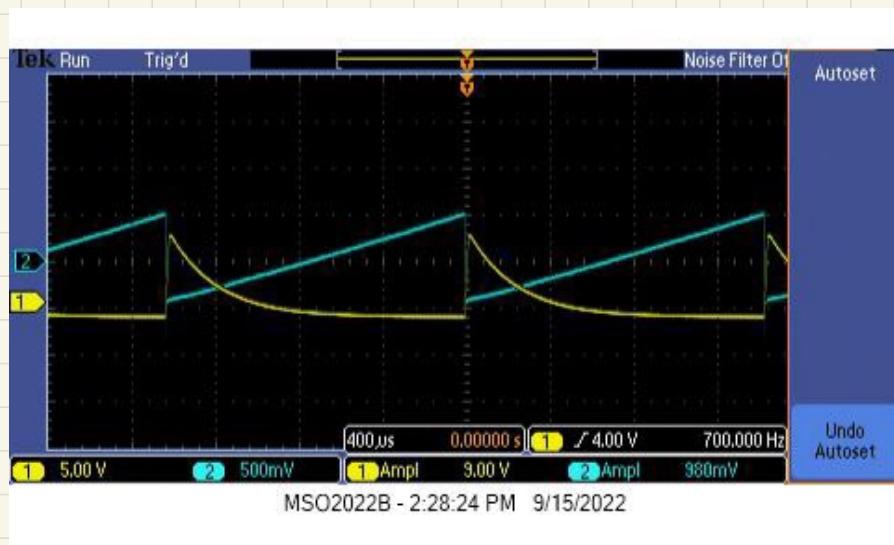

1 kHz

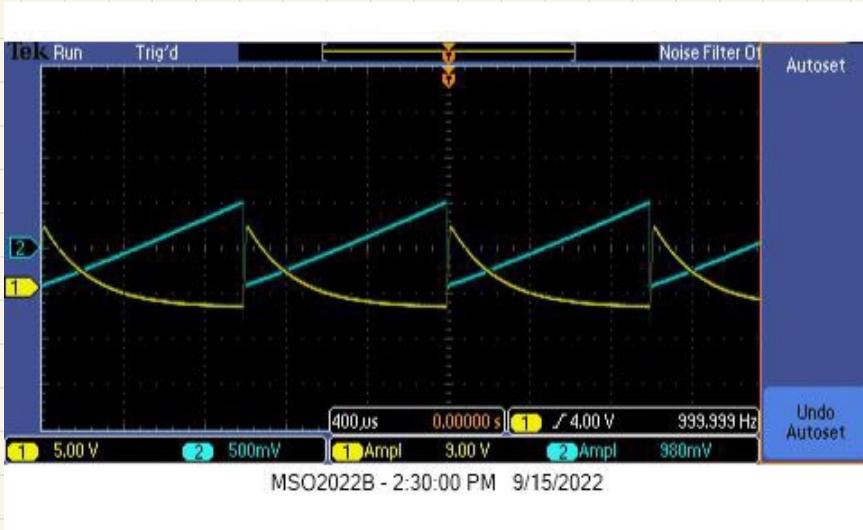


10 kHz

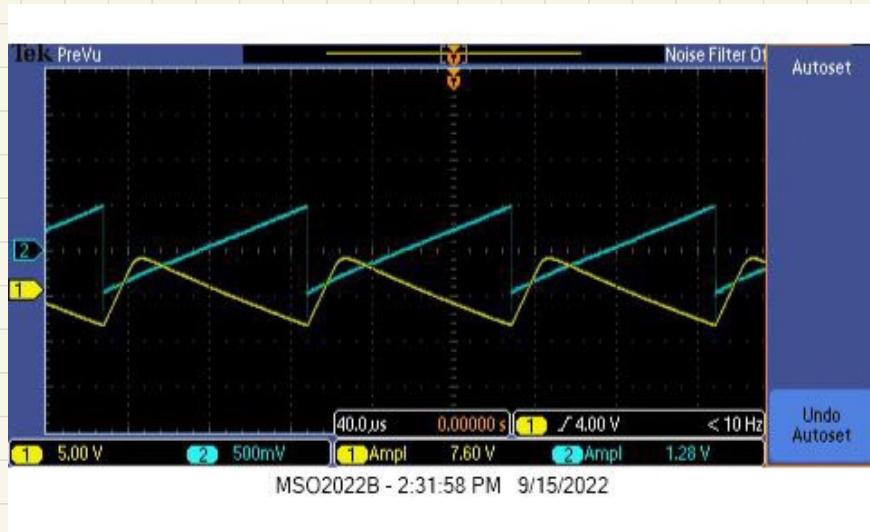

Vary the input frequency until the output reaches 70% of its high frequency magnitude.

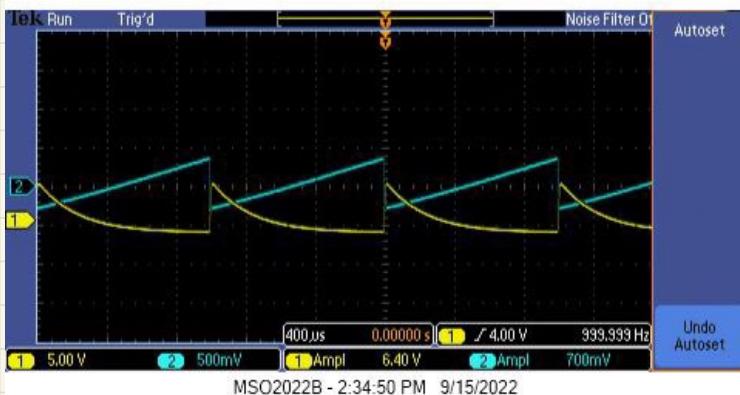
$$20 \log_{10} (A) = -3 \text{ dB}, A = 0.707$$



find the 3dB frequency.

We used 1 kHz

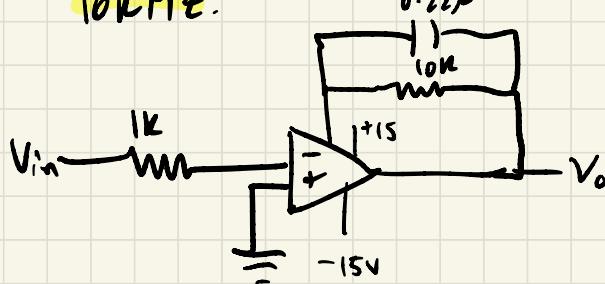f) The circuit shown below is constructed. A $0.5\text{V}_{\text{p-p}}$ square wave was applied. The output is then captured with frequencies of 10Hz , 100Hz , 500Hz , 700Hz , 1kHz , 10kHz .



10Hz